

DESIGN PROCEDURE FOR AN INTEGRATOR

By

Bhagyashri Tanaji Thorat

Assistant Professor


DESIGN PROCEDURE FOR AN INTEGRATOR

- If gain is not given in problem statement assume gain =10
- From the value of gain. Assume R_1 & calculate R_F
- Calculate f_a from f_b
- $f_a = f_b/10$
- Calculate C_F from the value of f_a
- Calculate $R_{Comp} = R_1 \parallel R_F$

PROBLEM STATEMENT TO DESIGN INTEGRATOR

Design a practical Integrator circuit to properly process input sinusoidal waveform upto 1kHz . The input amplitude is 10 mV.

CIRCUIT DIAGRAM INTEGRATOR

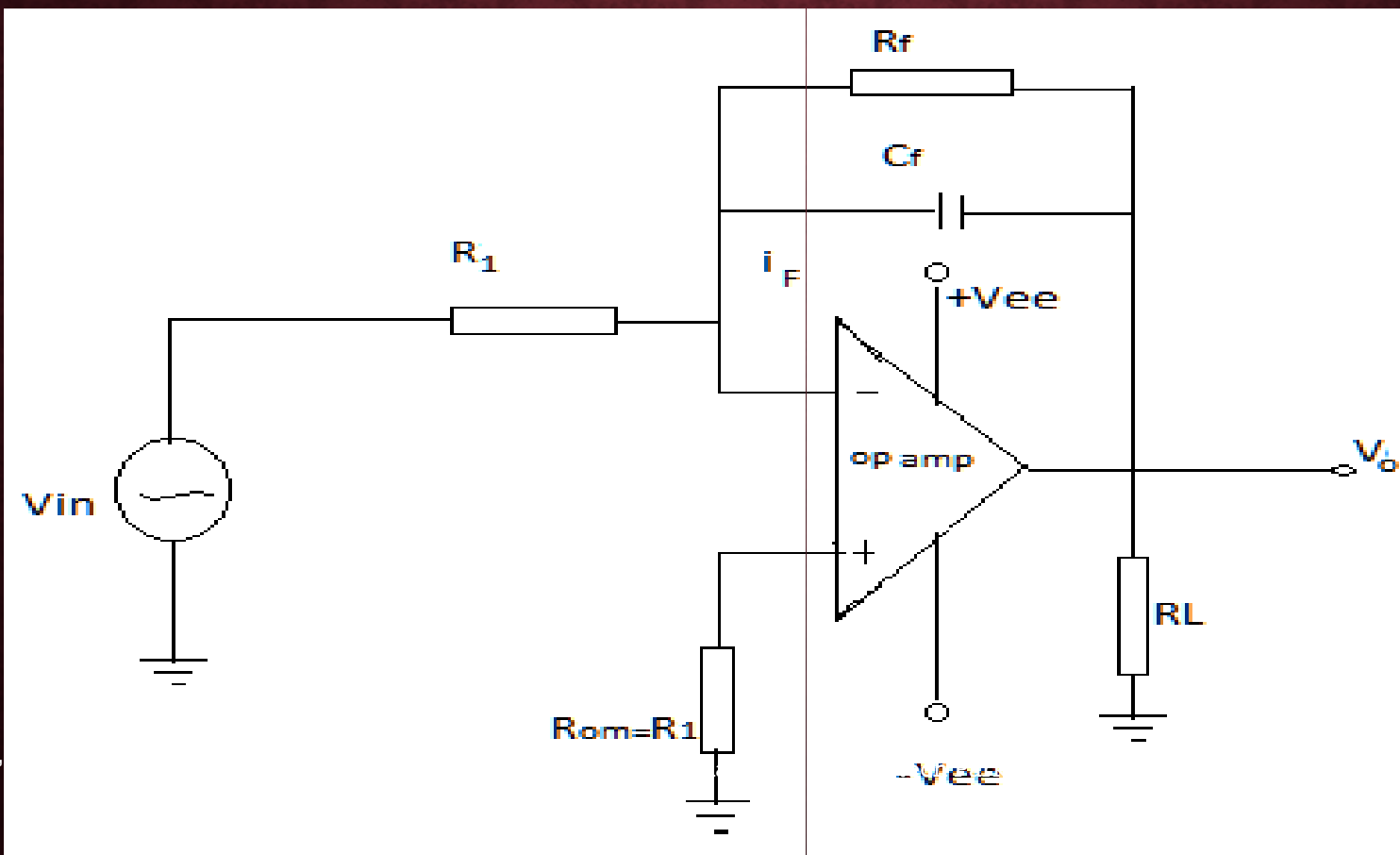

SOLUTION

- Given $f = 1 \text{ kHz}$; $V_i = 10 \text{ mV}$
- $\therefore f_b = 1 \text{ kHz}$
- Assume dc gain 10
- $f_b \geq 10 f_a$ & $f_a \leq 100 \text{ Hz}$
- $f_a = \frac{1}{2\pi R_F C_F} \quad R_F C_F = \frac{1}{2 \times 3.14 \times 100 \text{ Hz}} = 1.59 \times 10^{-3}$

SOLUTION

- $\frac{R_F}{R_1} = 10 \therefore R_1 = 10 \text{ k}\Omega \text{ \& } R_F = 100 \text{ k}\Omega$
- Substituting value of R_F
- $C_F = \frac{1.59 \times 10^{-3}}{100 \times 10^3} = 15.91 \text{ nF}$

SOLUTION

Calculate $R_{Comp} = R_1 \parallel R_F = 10\text{ k}\Omega \parallel 100\text{ k}\Omega \approx 10\text{ k}\Omega$